

# Insulators and Conductors




## Equipment Needed:

bulb



bulb holder

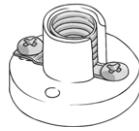


battery (cell)




battery holder




3 wires with crocodile clips

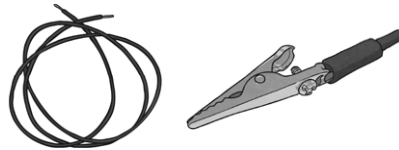

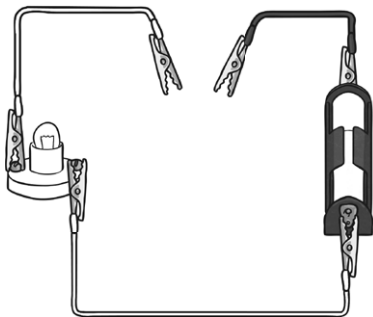Remember to set up your circuit like this:



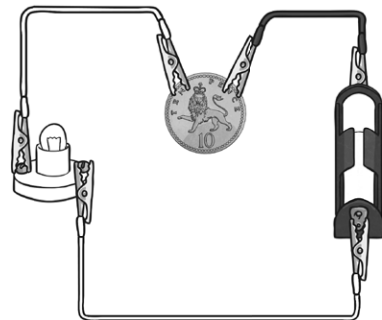When you add the material to test if it is a conductor or an insulator, it should look like this:



Test different materials and record your findings in the table below:

Conductors	Insulators